

Design assignment-2

2-stage OTA

Name- Aryan Kumar

Roll No. - 230108010

Branch - EEE

of _____
given with.

$$V_{tn} = 0.87V \quad V_{tp} = 0.39V \quad \mu_n C_{ox} = 230 \frac{\mu A}{V^2} \quad \mu_p C_{ox} = 100 \frac{\mu A}{V^2}$$

$$V_{dd} = 1.8V$$

$$L_{min} = 0.18 \mu m, \quad W_{min} = 0.2 \mu m$$

assumptions

$$V_{oo} = 200mV$$

$$(DC \text{ gain}) A_{DC} \geq 1000 \text{ or } 60dB$$

$$\text{Slew rate} \geq 10 V/\mu sec$$

$$C_L = 5pF$$


Specifications

$$\text{Phase margin (PM)} \geq 60^\circ$$

$$GBW = 5MHz$$

$$ICMR(+) = 1.6V$$

$$ICMR(-) = 0.8V$$

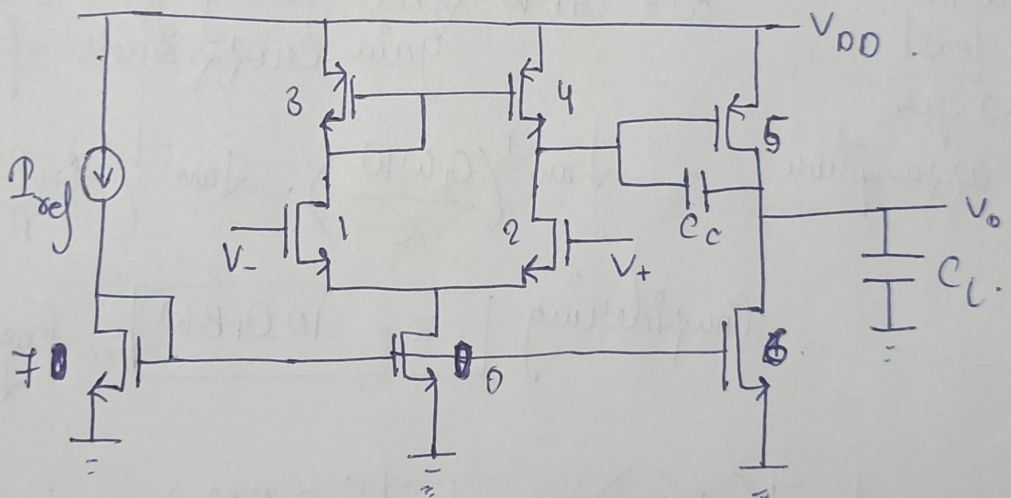

→ $\left(\frac{W}{L}\right)$ of M_1, M_2 is found using GBW .

→ $\left(\frac{W}{L}\right)$ of M_3, M_4 is found using $ICMR(+)$.

→ $\left(\frac{W}{L}\right)$ of M_5 is found using $ICMR(-)$.

→ I_{ref} is found using Slew rate.

→ $\left(\frac{W}{L}\right)$ of M_6 using phase Margin & Zero Location.

→ $\left(\frac{\omega}{1}\right)$ of M_z by M_s (related)

→ C_c using C_L & phase Margin.

Calculations

for $PM \geq 60^\circ$; $C_c \geq 0.22 C_L$.

Since OTA is 2nd order system it can be of type

$$\frac{V_o}{V_{i,m}} = \frac{A_{DC} (1 - s/z)}{(1 + s/p_1)(1 + s/p_2)}$$

$p_1, p_2 \rightarrow$ poles of system

$z \rightarrow$ zero of system

$$\angle \frac{V_o}{V_{i,m}} = -\tan^{-1}\left(\frac{\omega}{z}\right) - \tan^{-1}\left(\frac{\omega}{p_1}\right) - \tan^{-1}\left(\frac{\omega}{p_2}\right)$$

Should be at least 60° for our assumption

$\omega = GBW$ for unity gain or is gain crossover frequency.

$$= -\tan^{-1}\left(\frac{GBW}{z}\right) - \tan^{-1}\left(\frac{GBW}{p_1}\right) - \tan^{-1}\left(\frac{GBW}{p_2}\right)$$

Considering $z = 10 GBW$ for zero to be far apart.

$$= \tan^{-1}\left(\frac{GBW}{10 GBW}\right) - \tan^{-1}\left(\frac{GBW}{p_1}\right) - \tan^{-1}\left(\frac{GBW}{p_2}\right)$$

as we know $GBW = \frac{g_{m1}}{C_c}$

$$z = \frac{g_{m6}}{C_c}$$

$$p_2 = \frac{g_{m6}}{C_{OL}}$$

$$A_{DC} = (g_{m1} g_{m6}) R_2 \left[\frac{1}{g_{m6} (r_{o6} || r_{o7}) g_{m1} (r_{o2} || r_{o4}) C_c} \right]$$

$$= -\tan^{-1}\left(\frac{1}{10}\right) - \tan^{-1}\left(\frac{g_{m1} \times g_{m6} R_1 R_2}{g_c}\right) - \tan^{-1}\left(\frac{GBW}{P_2}\right)$$

$$-180^\circ + PM = -\tan^{-1}\left(\frac{1}{10}\right) - \tan^{-1}(A_{DC}) - \tan^{-1}\left(\frac{GBW}{P_2}\right)$$

$$PM = 180^\circ - 5.71 - 90^\circ - \tan^{-1}\left(\frac{GBW}{P_2}\right)$$

$$PM = 84.29 - \tan^{-1}\left(\frac{GBW}{P_2}\right)$$

$$60^\circ = 84.29 - \tan^{-1}\left(\frac{GBW}{P_2}\right)$$

$$24.29 = \tan^{-1}\left(\frac{GBW}{P_2}\right)$$

$$\frac{GBW}{P_2} = 0.4813 \Rightarrow P_2 = 2.2 GBW$$

$$\pi = 10 GBW$$

$$\frac{g_{m6}}{C_c} = 10 \frac{g_{m1}}{C_c}$$

$$\frac{g_{m6}}{C_L} \geq 2.2 \frac{g_{m1}}{C_c}$$

$$\frac{10 g_{m1}}{C_L} \geq 2.2 \frac{g_{m1}}{C_c}$$

$$\boxed{C_c \geq 0.22 C_L}$$

$$\text{if } C_L = 10 \text{ pF}$$

$$C_c \geq 2.2 \text{ pF}$$

$$\text{Let } C_c = 3 \text{ pF}$$

$$\text{Slew rate} = \frac{P_s}{C_c}$$

$$P_s = 10 \text{ V}/\mu\text{s} \times 3 \text{ pF} = 30 \mu\text{A}$$

So for M_1 & M_2 .

$$g_{m1} = \text{GBW} \cdot C_c \cdot 2\pi = 5 \times 10^6 \times 3 \times 10^{-12} \times 2\pi$$

$$= 94.24 \times 10^{-6} \text{ s} = 94.24 \mu\text{s}$$

$$P_s = \frac{1}{2} \mu_n C_{ox} \left(\frac{\omega}{l} \right) (V_{DD})^2$$

$$g_{m1} = \sqrt{2 P_s \mu_n C_{ox} \left(\frac{\omega}{l} \right)_1}$$

$$\frac{g_{m1}^2}{2 P_s \mu_n C_{ox}} = \left(\frac{\omega}{l} \right)_1$$

$$\left(\frac{\omega}{l} \right)_{1,2} = \frac{(94.24 \mu)^2}{230 \times 10^{-6} \times 30 \times 10^{-6}}$$

$$= \frac{8881.1776 \times 10^{-12}}{10 \times 230 \times 10^{-6} \times 30 \times 10^{-6}} = 1.287$$

$$\sim 2$$

So for M_3 & M_4 .

$$\left(\frac{\omega}{l} \right)_{3,4} = \frac{2 P_{D3}}{\mu_p C_{ox} [V_{DD} - 1 \text{CMR}(+) - V_{t3} + V_{t1}]^2}$$

$$= \frac{30 \times 10^{-6}}{100 \times 10^{-6} [1.8 - 1.6 - 0.39 + 0.37]^2}$$

$$= 9.259$$

$$\sim 10$$

Since $ICMR(+)=V_{DD}-\sqrt{\frac{P_s}{\beta_3}}-V_{t3,max}+V_{t1,min}$

at $ICMR(+)-V_{t1,min}<V_{G3}$

$$V_{G3}=V_{DD}-V_{DD3}-V_{tp}$$

for M_0 & M_{07}

$$V_{D(sat)_0}=ICMR(-)-V_{SS}-\sqrt{\frac{P_s}{\beta_1}}-V_{th,max}$$

$$\therefore ICMR(-)-V_{DD1}-V_{th,max}=V_{D(sat)_0}$$

$$(V_{SS}=0)$$

$$V_{D(sat)_s}=0.8-0.319-0-0.88$$

$$=0.1$$

$$\left(\frac{W}{L}\right)_{00}=\frac{2P_s}{\mu_m C_{ox}(V_{D(sat)_0})^2}=\frac{2 \times 30}{230 \times (0.1)^2}$$

$$\left(\frac{W}{L}\right)_{0,07}=26$$

$$=26.0$$

$$\sim 26$$

for M_{05}

$$g_{m_{05}}=10g_{m1}=942.4 \mu$$

$$g_{m_4}^2=2P_4 \mu_p C_{ox} \left(\frac{W}{L}\right)_4$$

$$g_{m_4}=\sqrt{2 \times 15 \times 100 \times 10 \times 10^{-6} \times 10^{-6}}$$

$$=173.2 \mu$$

Since M_4 & M_{05} have equal overdrives.

$$\left(\frac{\omega}{L}\right)_{05} = \frac{g_{m6} \times \left(\frac{\omega}{L}\right)_4}{g_{m4}}$$

$$\left(\frac{\omega}{L}\right)_{05} = \frac{942.4 \times 10^{-6} \times 10}{173.2 \times 10^{-6}}$$

$$= 54.41 \sim 55.$$

for M_{06} \swarrow equal P_{06}

$$P_{05} = \frac{\left(\frac{\omega}{L}\right)_{05} \times P_4}{\left(\frac{\omega}{L}\right)_4} = \frac{55 \times 15 \times 10^{-6}}{10}$$

$$= 82.5 \mu A.$$

$$\left(\frac{\omega}{L}\right)_{06} = \frac{P_7 \times \left(\frac{\omega}{L}\right)_{00}}{P_{05}} = \frac{82.5 \times 10^{-6} \times 26}{30 \times 10^{-6}}$$

$$= 71.5 \sim 72.$$

Now for No Systematic effects.

$$\frac{2 \times \left(\frac{\omega}{L}\right)_{06}}{\left(\frac{\omega}{L}\right)_{00}} = \frac{\left(\frac{\omega}{L}\right)_{05}}{\left(\frac{\omega}{L}\right)_4} \overset{\text{if}}{\text{Satisfied}}$$

$$= 5.5.$$

$$I_{dc} = 30 \mu A$$

$$C_c = 3 pF$$

$$C_L = 10 pF$$

Since $L_{min} = 180 nm$.

Initial Values

Considering $L = 180 nm$

$$M_{1,2} \cdot g_{m_{1-2}} =$$

$$W = 360 nm$$

$$L = 180 nm \quad \sigma_{01-2} =$$

$$M_{3,4} \cdot g_{m_{3-4}} =$$

$$W = \cancel{4.6} \mu m$$

$$L = 180 nm \quad \sigma_{03-4} =$$

$$M_0 \cdot g_{m_0} =$$

$$W = \cancel{4.6} \mu m$$

$$L = 180 nm \quad \sigma_{00} =$$

$$M_{05} \cdot g_{m_{05}} =$$

$$W = \cancel{21.5} \mu m$$

$$L = 180 nm \quad \sigma_{05} =$$

$$M_{06} \cdot g_{m_{06}} =$$

$$W = \cancel{8.6} \mu m$$

$$L = 80 nm \quad \sigma_{06} =$$

$$M_{07} \cdot$$

$$W = \cancel{4.6} \mu m$$

$$L = 180 nm$$

for these values I - got gain of 55 dB after fine tuning it.

$$M_{1-2}$$

$$W = 1.8 \mu m$$

$$L = 180 nm$$

$$M_{3-4}$$

$$W = 2.2 \mu m$$

$$L = 180 nm$$

$$M_0$$

$$W = 8 \mu m$$

$$L = 180 nm$$

$$M_5$$

$$W = 25 \mu m$$

$$L = 180 nm$$

$$M_6$$

$$W = 23 \mu m$$


$$L = 180 nm$$

$$M_7$$

$$W = 5 \mu m$$


$$L = 180 nm$$

for gain of 60

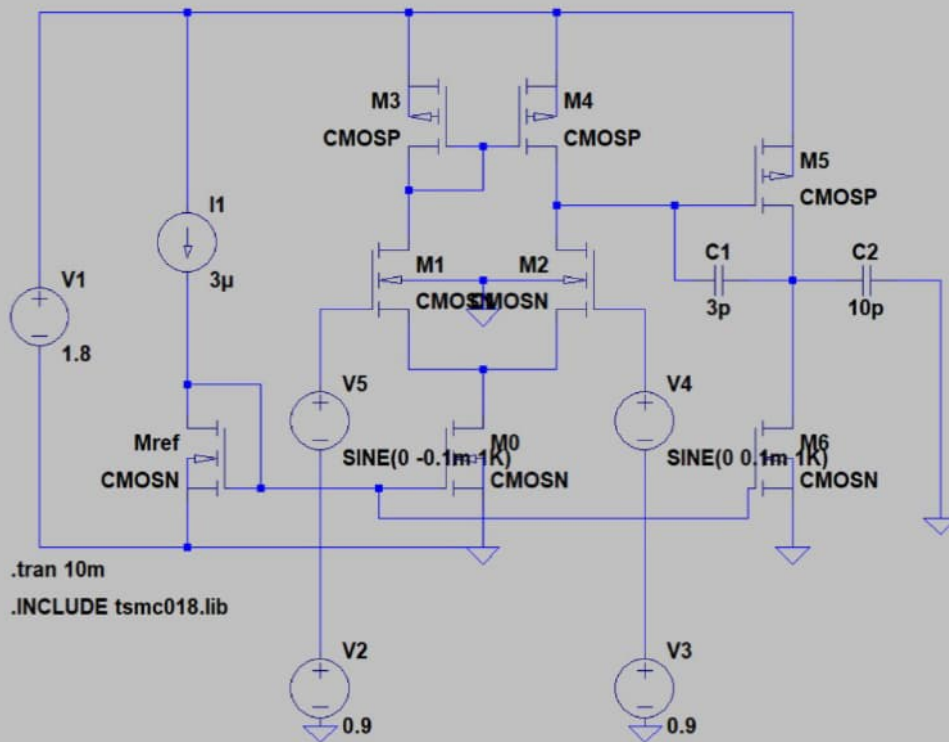





OTA[1]

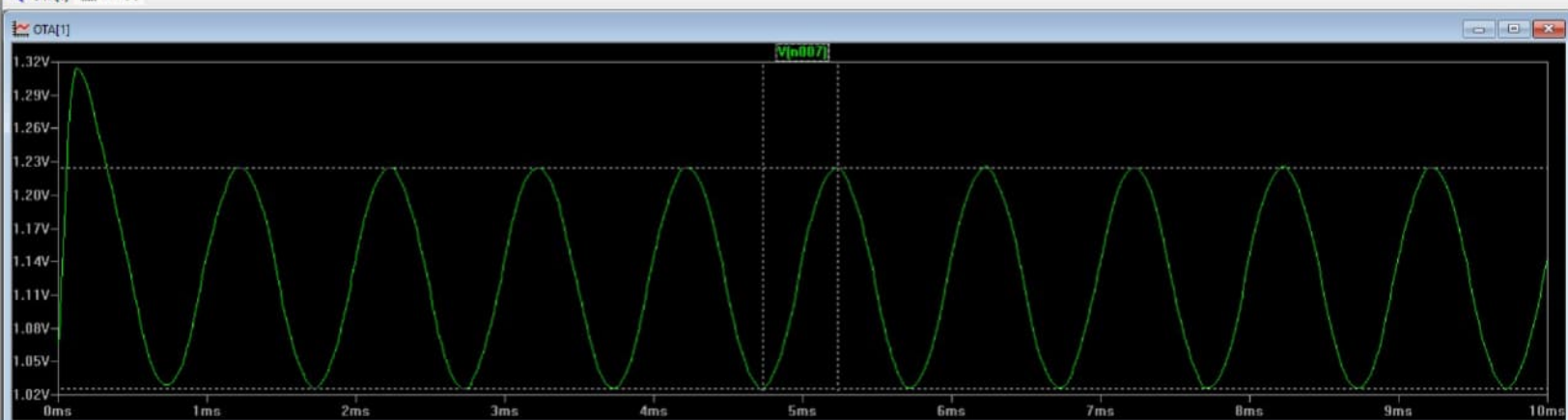

OTA[1]

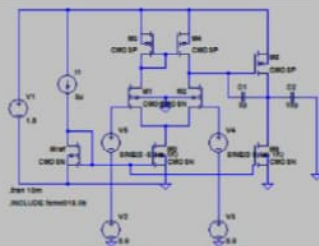

OTA[1]			
Cursor 1			
		V(n007)	
Horz	4.7310345ms	Vert	1.0252939V
Cursor 2			
		V(n007)	
Horz	5.2344820ms	Vert	1.2248673V
Diff (Cursor2 - Cursor1)			
Horz	503.44829us	Vert	199.57338mV
Freq	1.9863014KHz	Slope	396.413

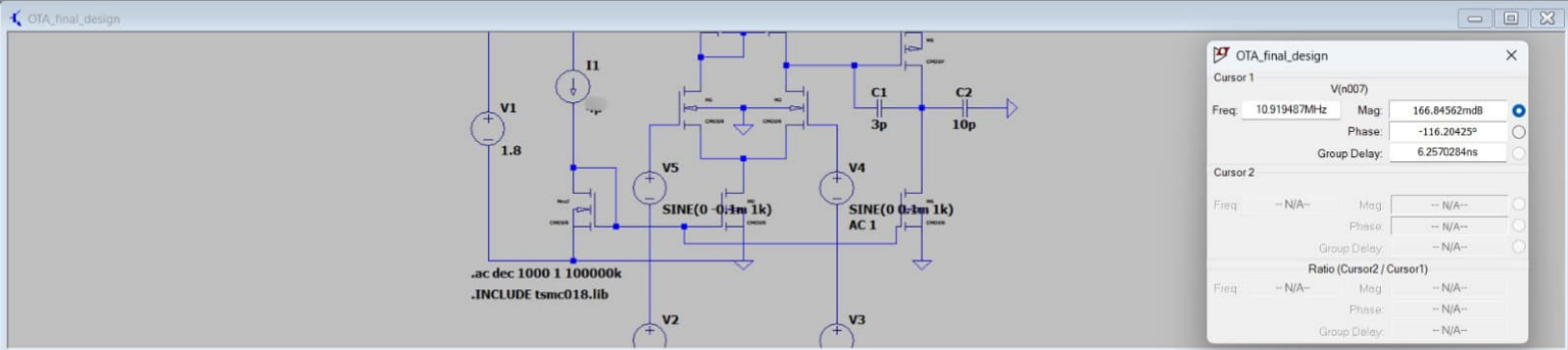

$$\tau_{01-2} = 4.7 \text{ K}\Omega g_{m_{1-2}} = 10^{-5} = 10 \mu s$$

$$\tau_{0,0} = 2.5 \text{ K}\Omega g_{m_0} = 2 \times 10^{-5} = 20 \mu s$$

$$\tau_{05} = 416 \Omega g_{m_5} = 0.12 \times 10^{-3} = 0.12 \text{ ms}$$

$$\tau_{0_{8-4}} = 4.7 \text{ K}\Omega g_{m_{8-4}} = 10^{-5} = 10 \mu s$$

$$\tau_{06} = 416 \Omega g_{m_6} = 0.12 \times 10^{-3} = 0.12 \text{ ms}$$

$$\tau_{07} = 3.34 \text{ K}\Omega g_{m_7} = 15 \mu s$$